



These were made with 2n3904 and 2n3906 transistors in mind... Most transistors should work, but mind the orientation. BC556, BC546, and other transistors would need flipped, so check before you solder. I also omitted one sandrode, because I found it unnecessary, it would be connected to the base of the NPN .

"A" and "B" are the sandrodes, the asterisk node is the output. The unmarked capacitors should all be of the same value. VCC is 9V, but a little higher or lower would probably also work.

